

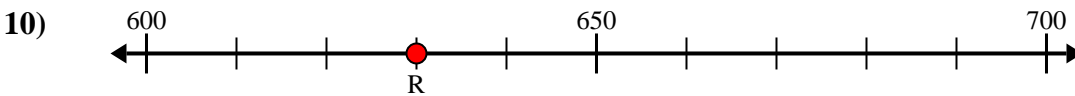
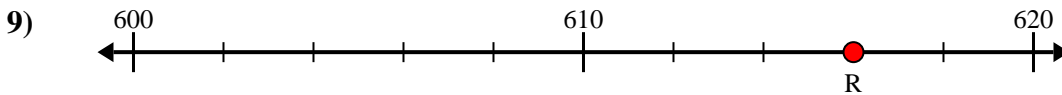
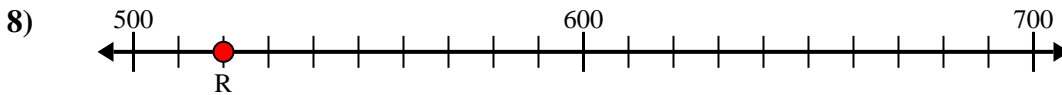
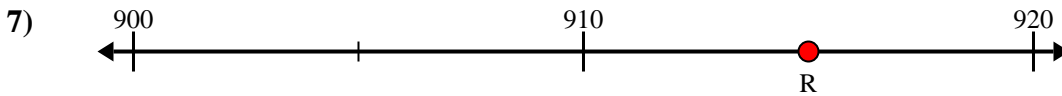
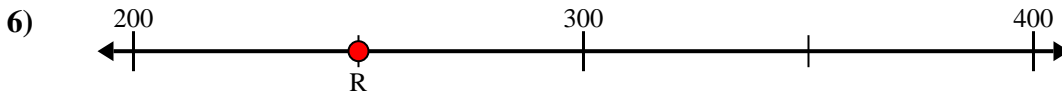
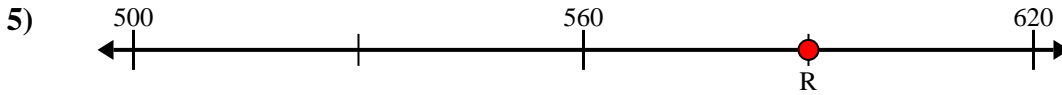
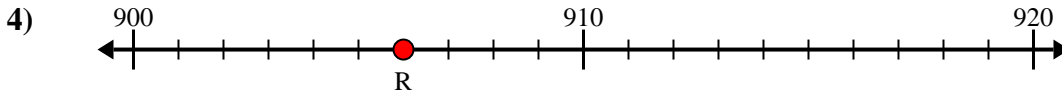
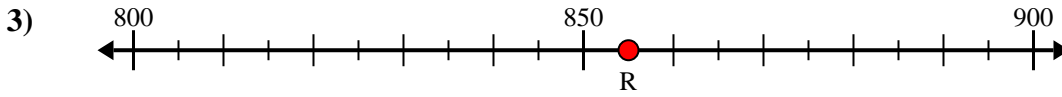


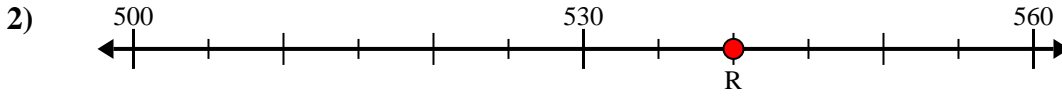

Encontrar el valor de R.










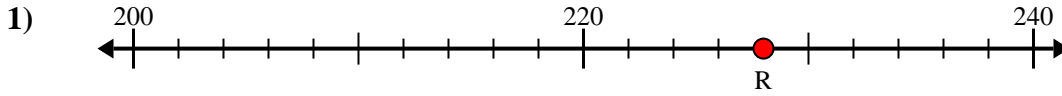


Respuestas

1. _____
2. _____
3. _____
4. _____
5. _____
6. _____
7. _____
8. _____
9. _____
10. _____



Encontrar el valor de R.

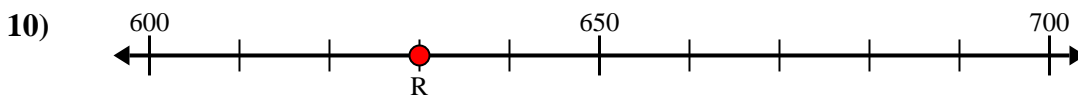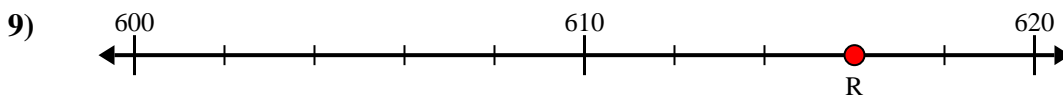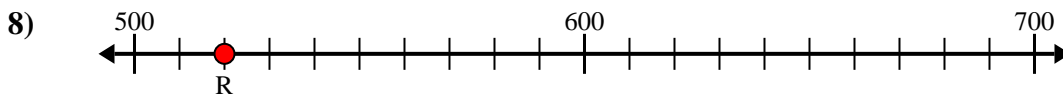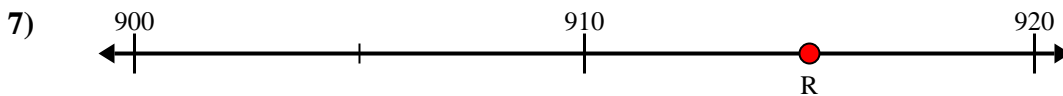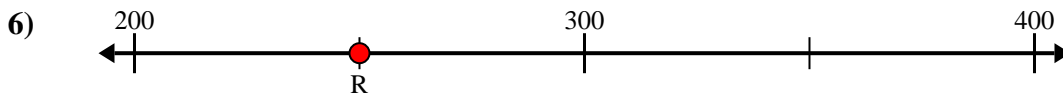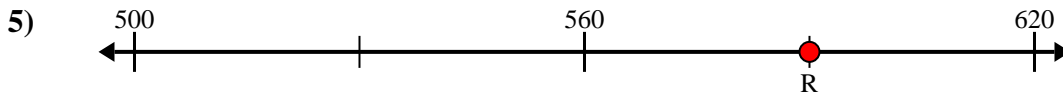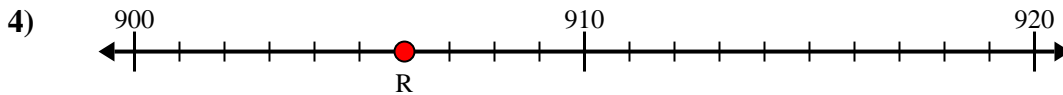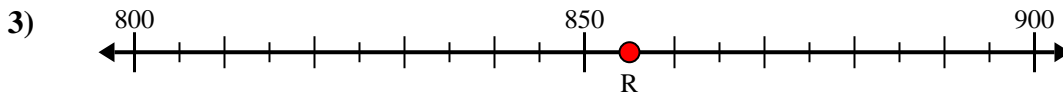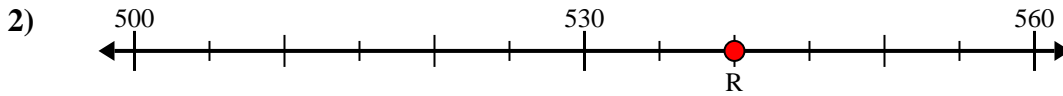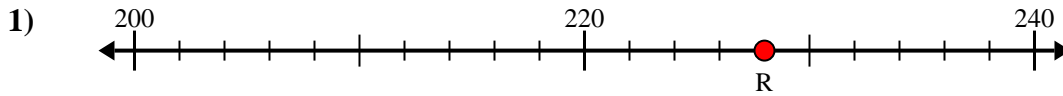

Respuestas

1. 228

2. 540

3. 855

4. 906

5. 590

6. 250

7. 915

8. 520

9. 616

10. 630