

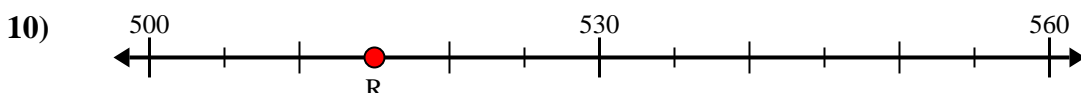
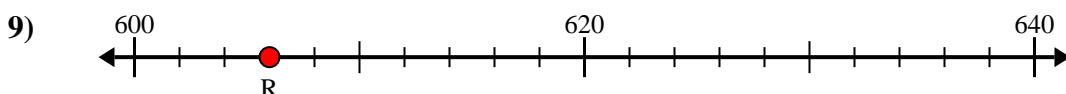
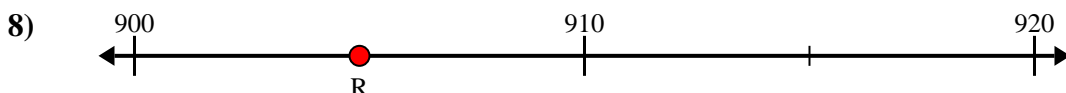
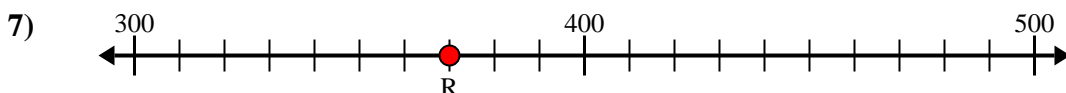
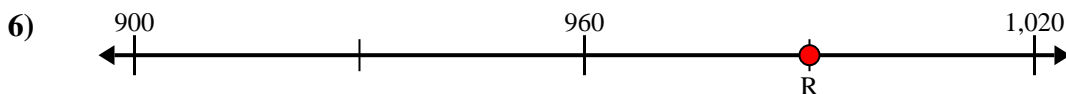
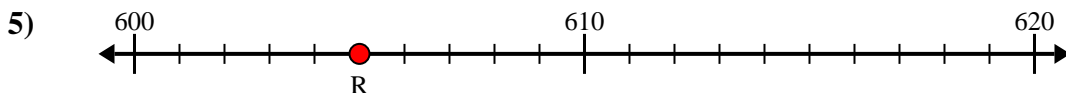
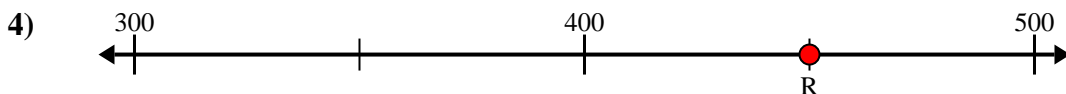
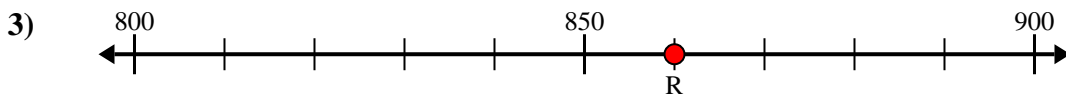


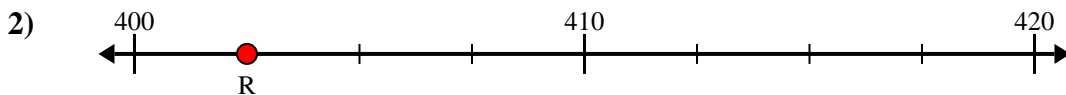

Encontrar el valor de R.

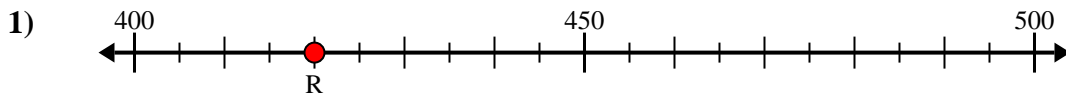

Respuestas

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Encontrar el valor de R.

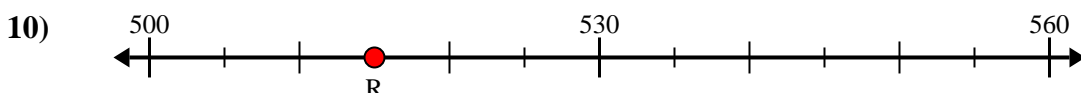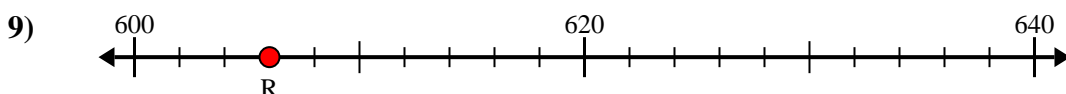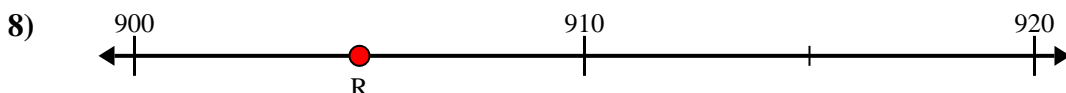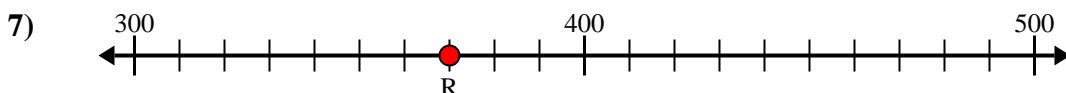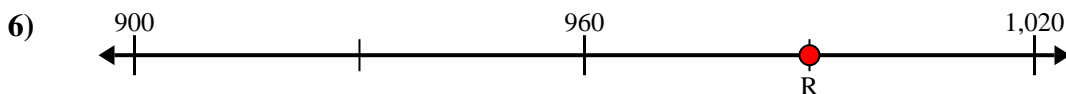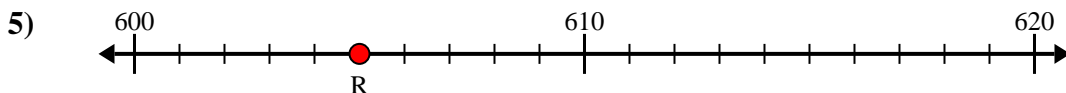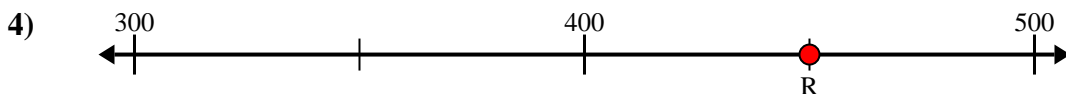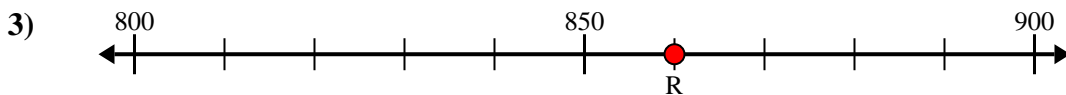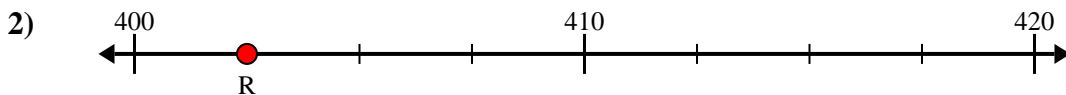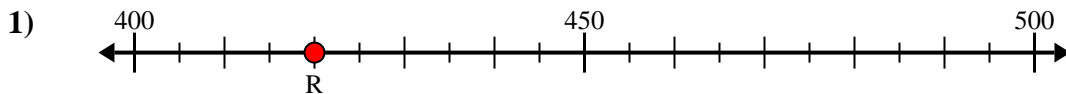

Respuestas

1. 420

2. 402.5

3. 860

4. 450

5. 605

6. 990

7. 370

8. 905

9. 606

10. 515