

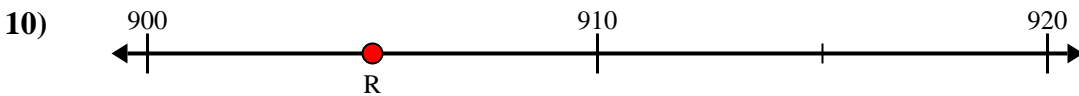
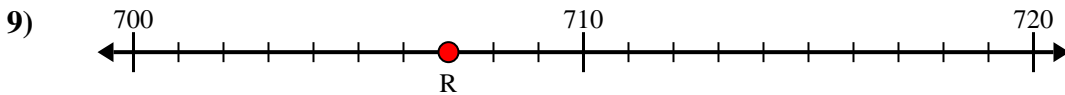
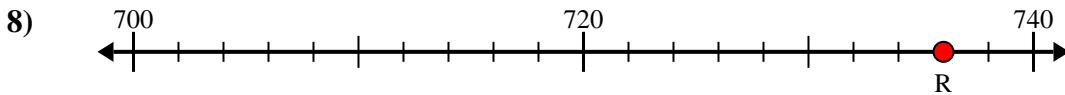
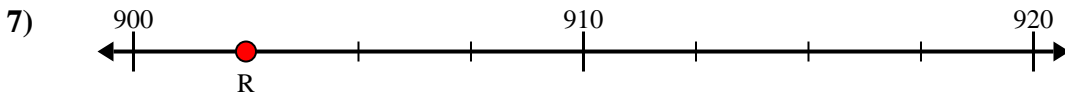
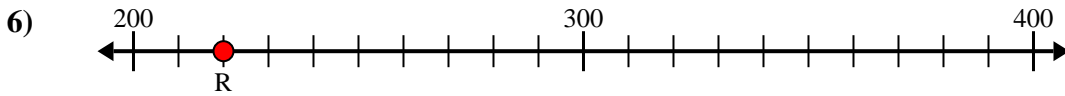
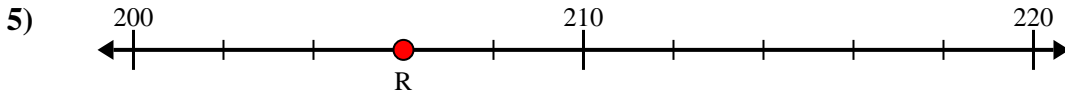
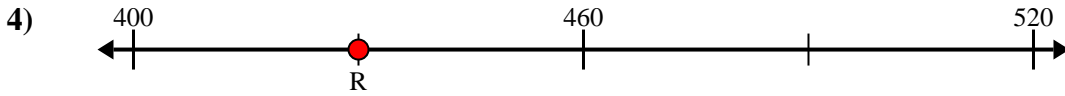
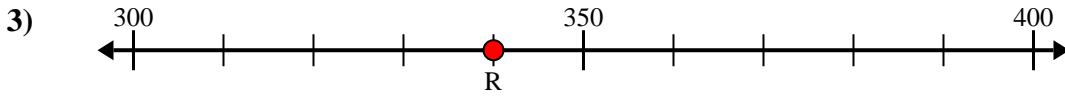


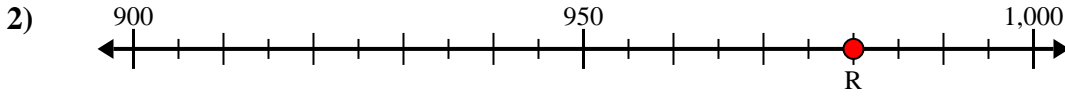

Encontrar el valor de R.

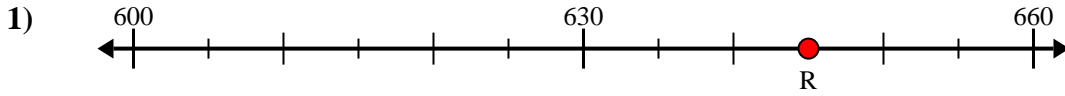

Respuestas

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Encontrar el valor de R.

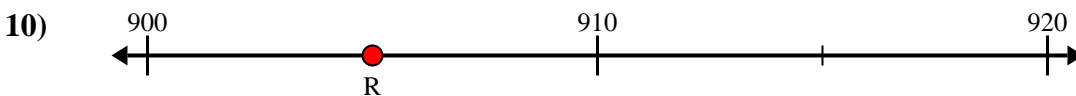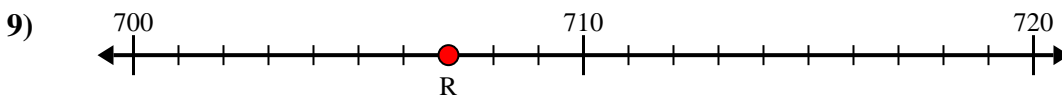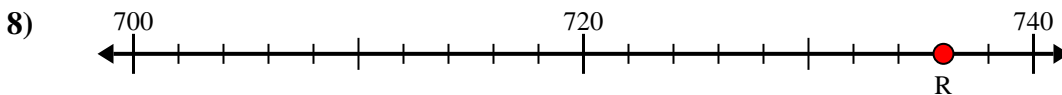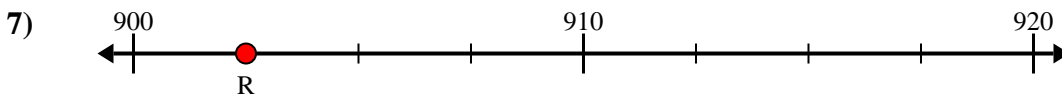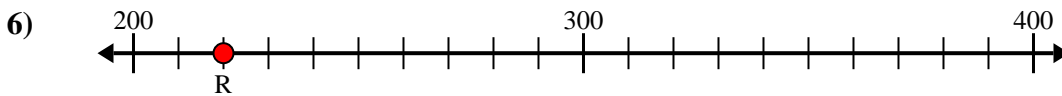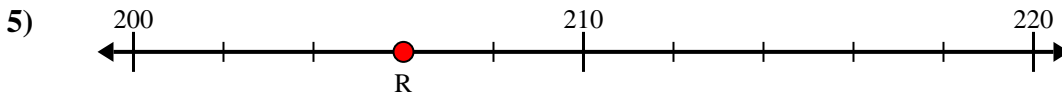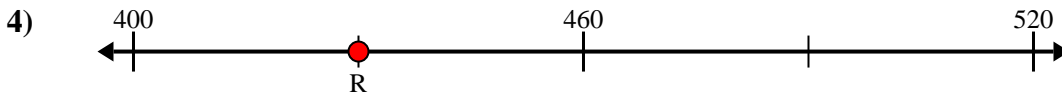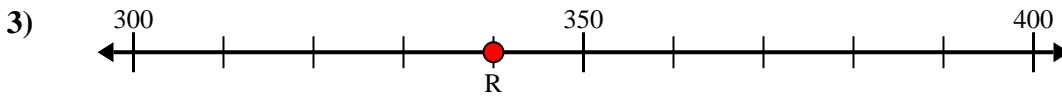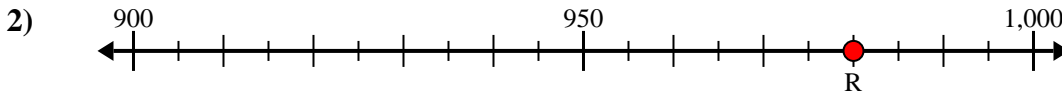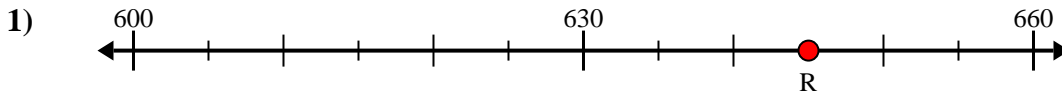

Respuestas

1. 645

2. 980

3. 340

4. 430

5. 206

6. 220

7. 902.5

8. 736

9. 707

10. 905