

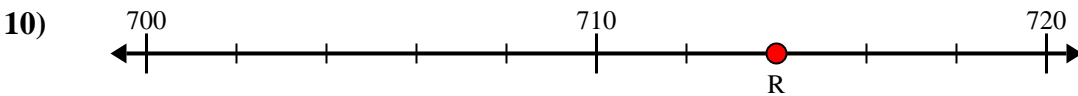
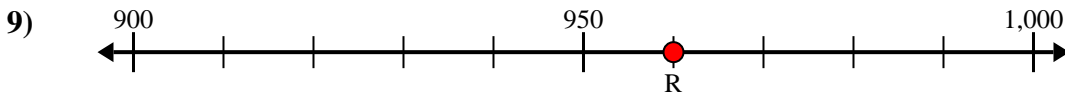
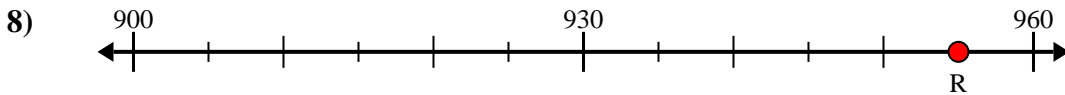
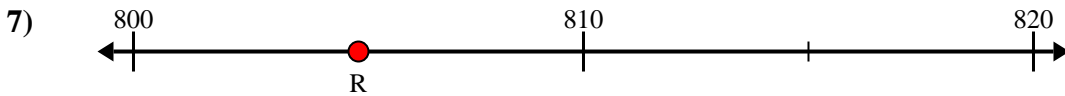
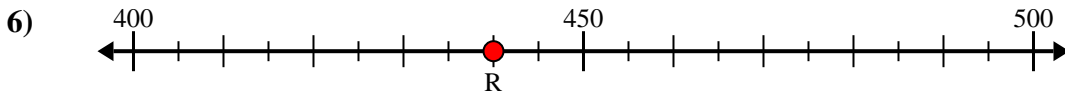
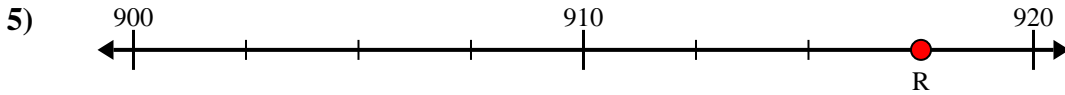
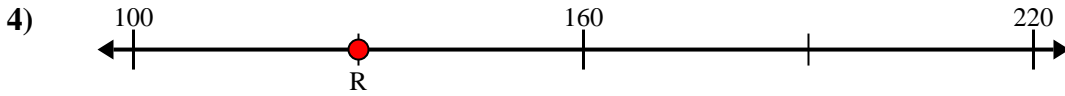
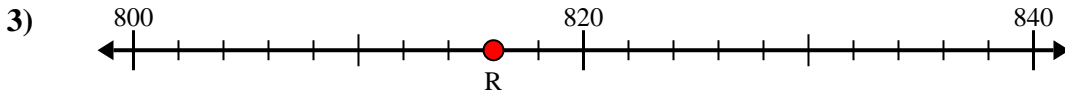


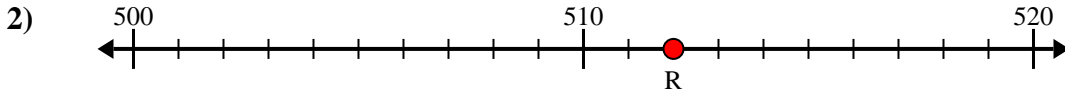

Encontrar el valor de R.

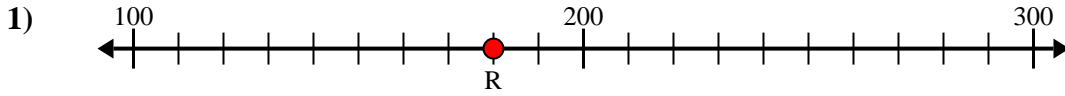

Respuestas

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Encontrar el valor de R.

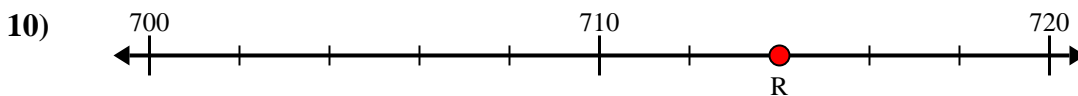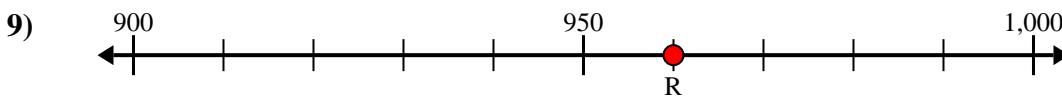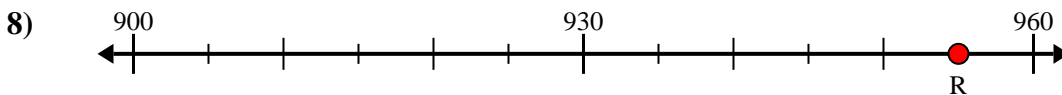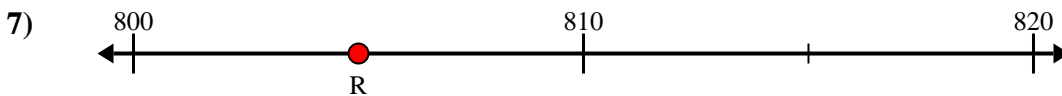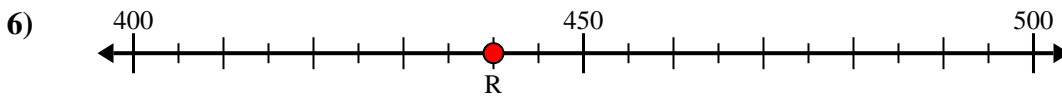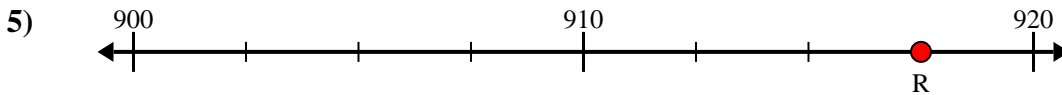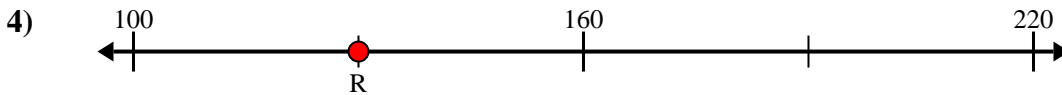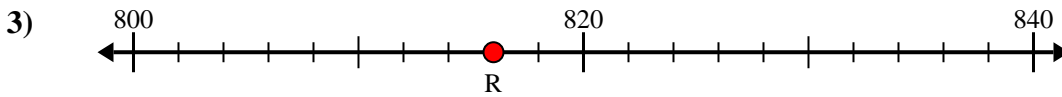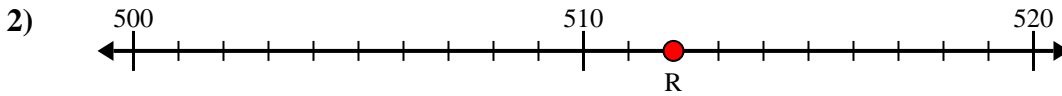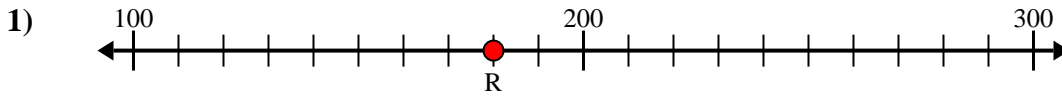

Respuestas

1. 180
2. 512
3. 816
4. 130
5. 917.5
6. 440
7. 805
8. 955
9. 960
10. 714