

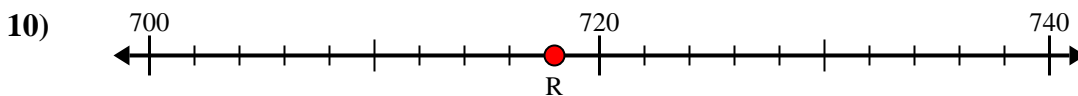
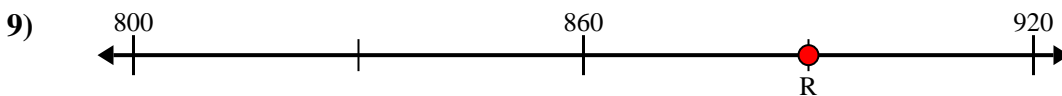
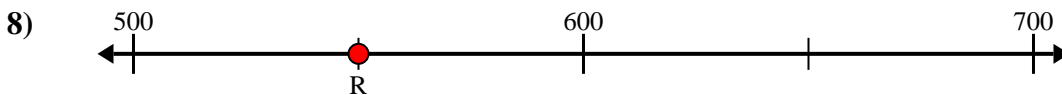
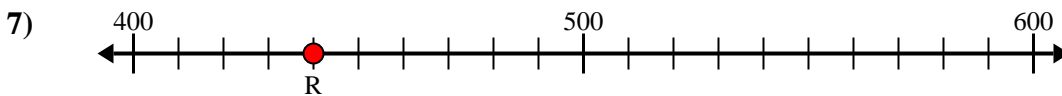
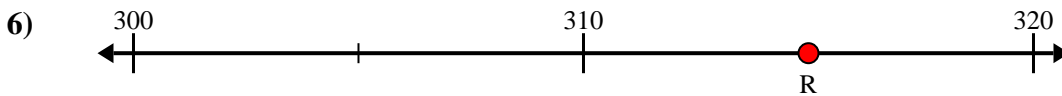
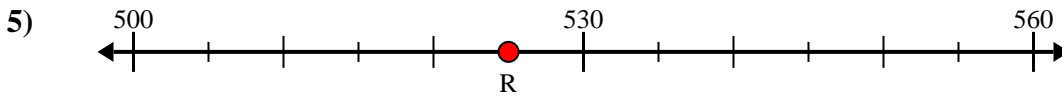
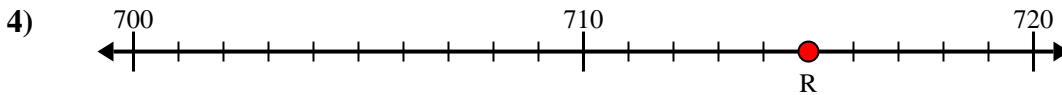
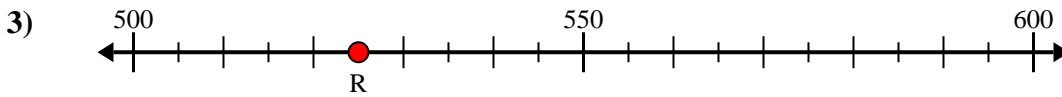


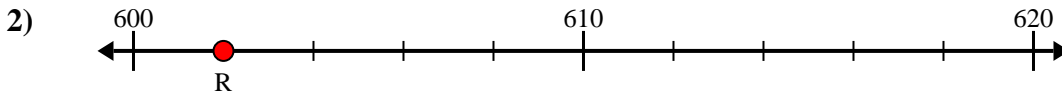

Encontrar el valor de R.










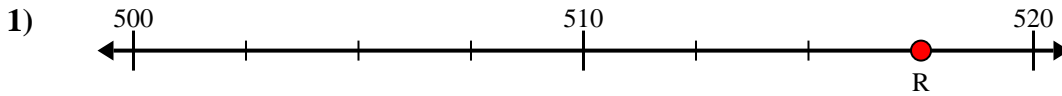


Respuestas

- 1. \_\_\_\_\_
- 2. \_\_\_\_\_
- 3. \_\_\_\_\_
- 4. \_\_\_\_\_
- 5. \_\_\_\_\_
- 6. \_\_\_\_\_
- 7. \_\_\_\_\_
- 8. \_\_\_\_\_
- 9. \_\_\_\_\_
- 10. \_\_\_\_\_



Encontrar el valor de R.

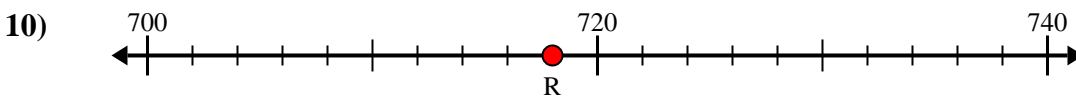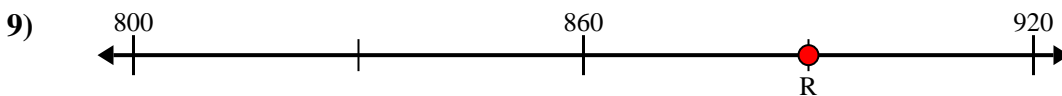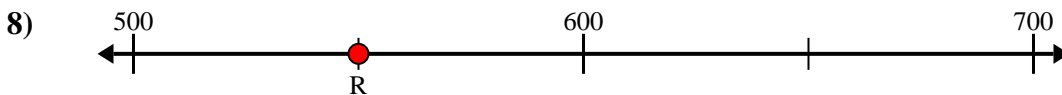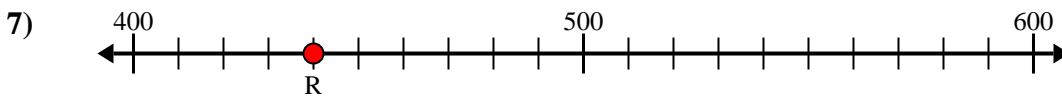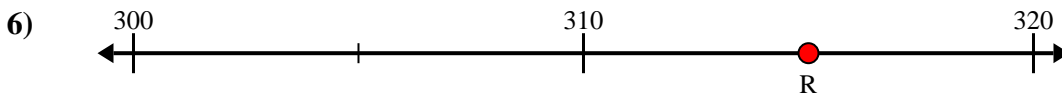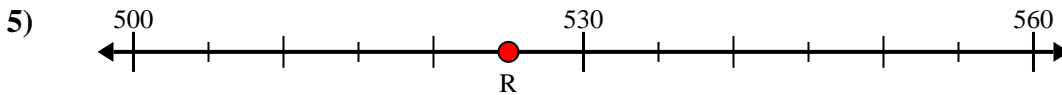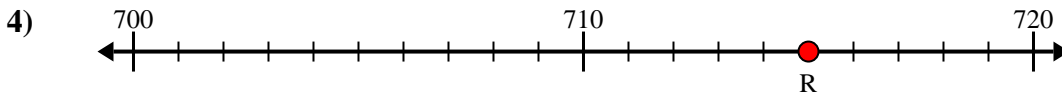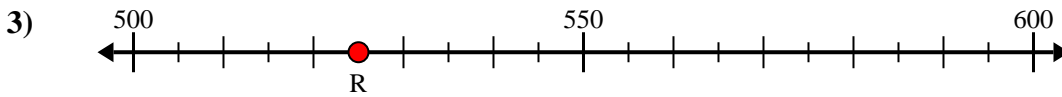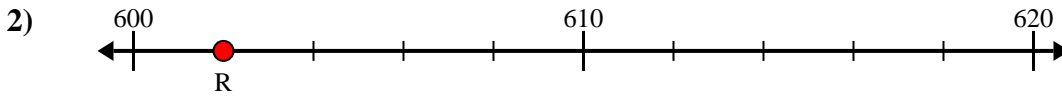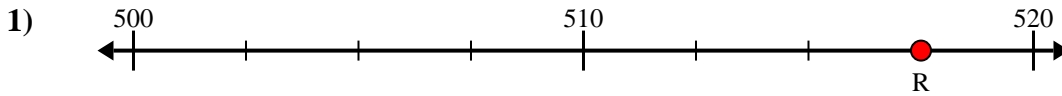

**Respuestas**

1. 517.5

2. 602

3. 525

4. 715

5. 525

6. 315

7. 440

8. 550

9. 890

10. 718