

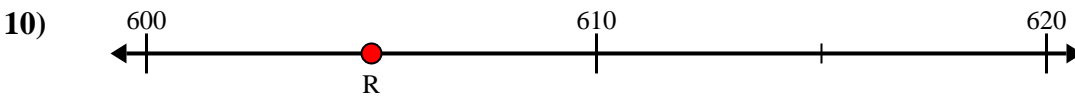
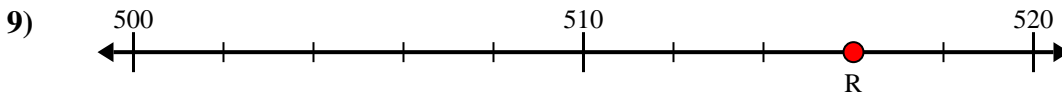
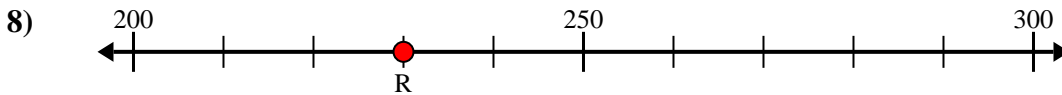
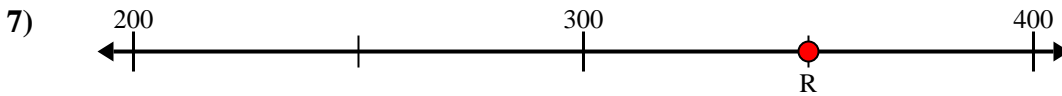
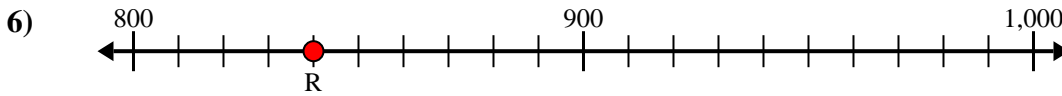
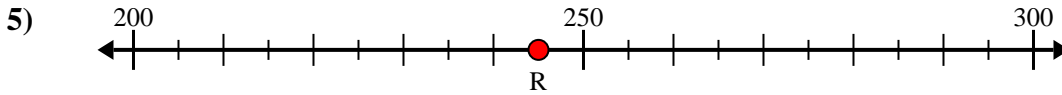
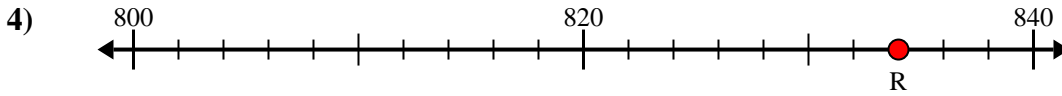
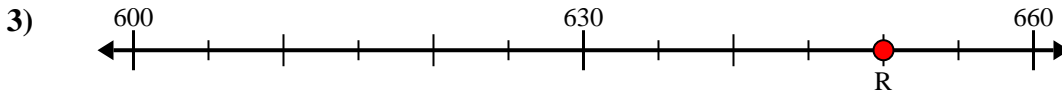


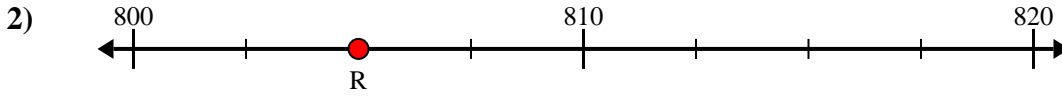

Encontrar el valor de R.

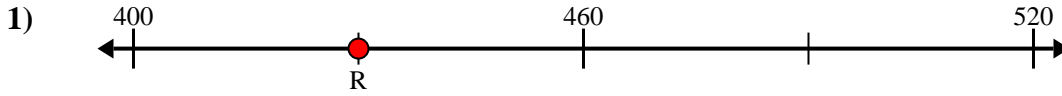

Respuestas

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Encontrar el valor de R.

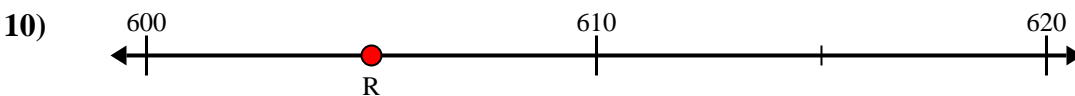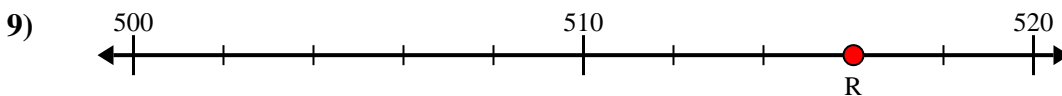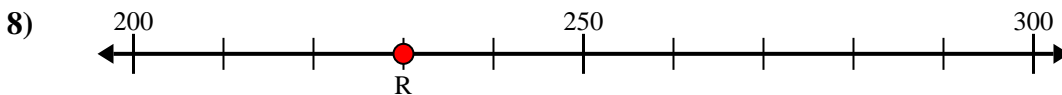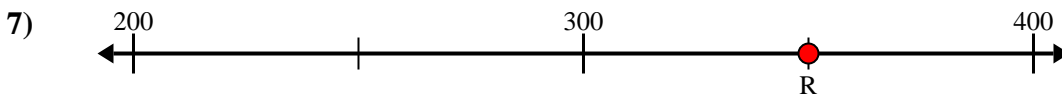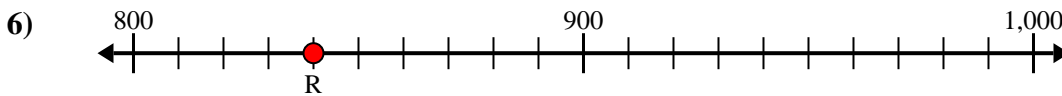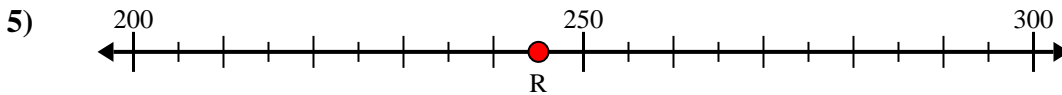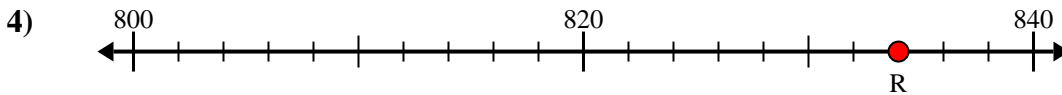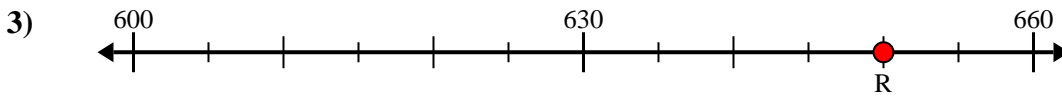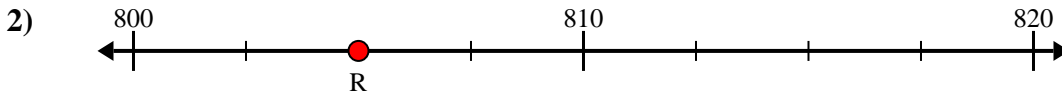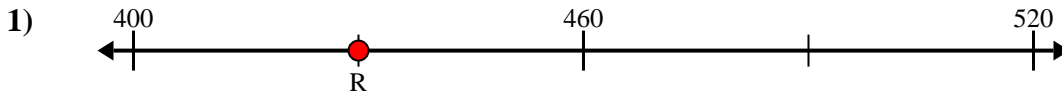

Respuestas

1. 430

2. 805

3. 650

4. 834

5. 245

6. 840

7. 350

8. 230

9. 516

10. 605