

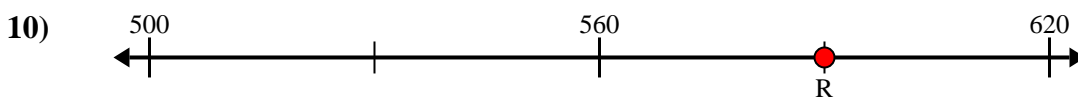
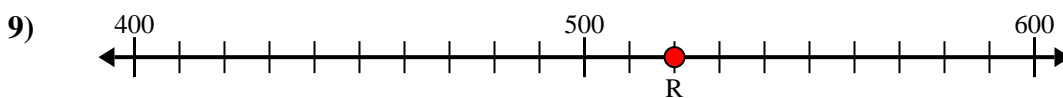
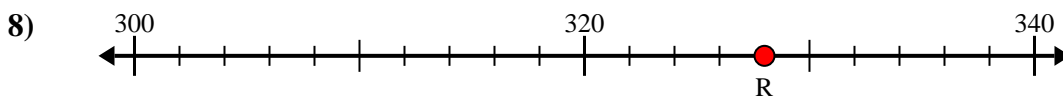
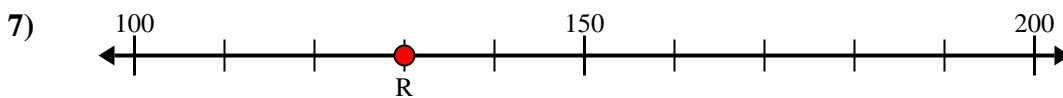
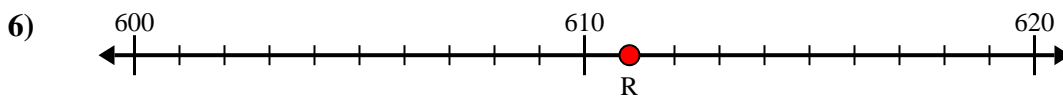
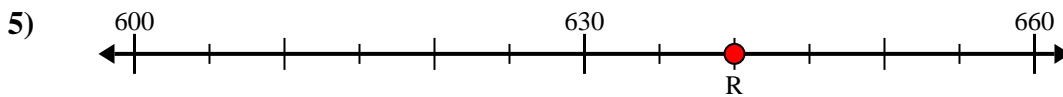
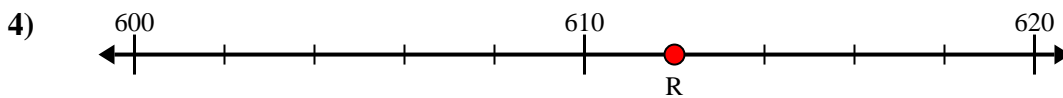
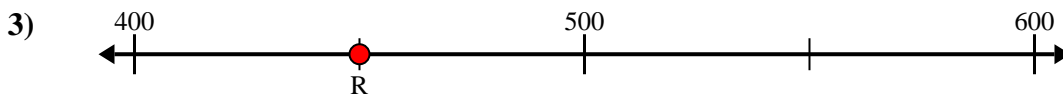


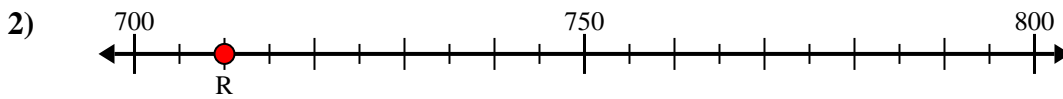

Encontrar el valor de R.

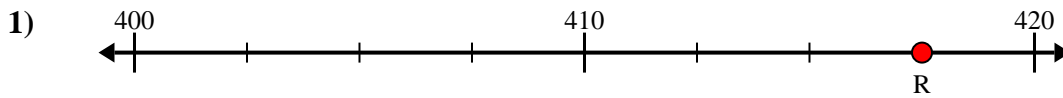

Respuestas

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Encontrar el valor de R.

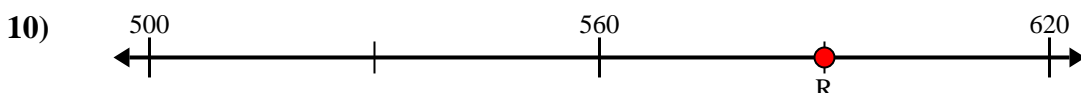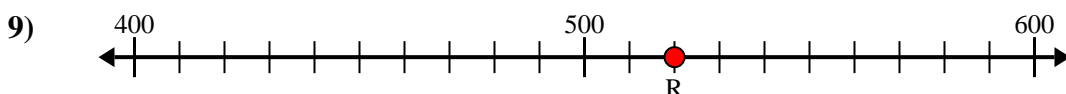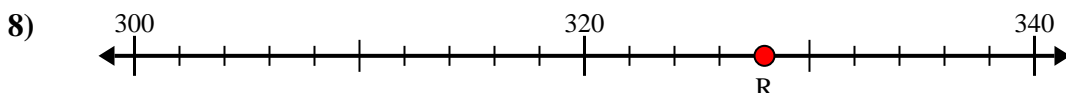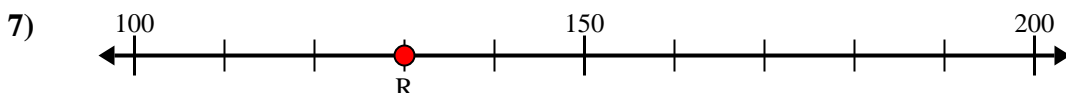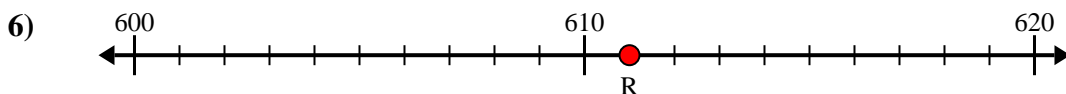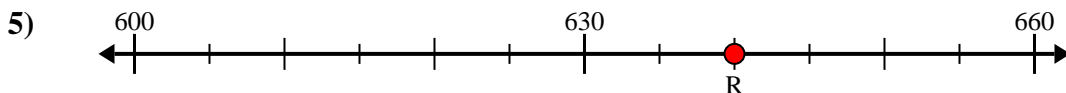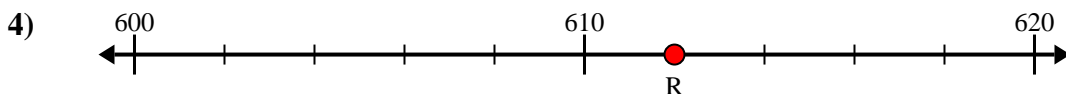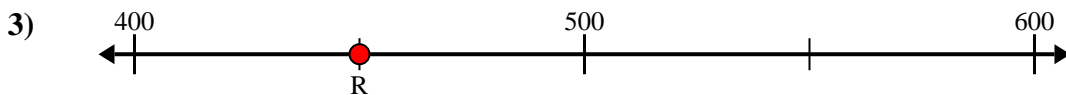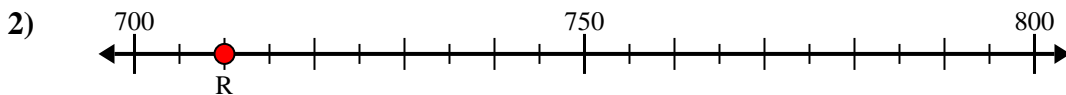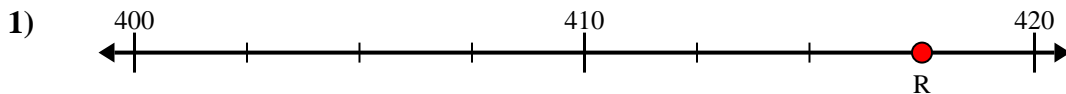

Respuestas

1. 417.5

2. 710

3. 450

4. 612

5. 640

6. 611

7. 130

8. 328

9. 520

10. 590