

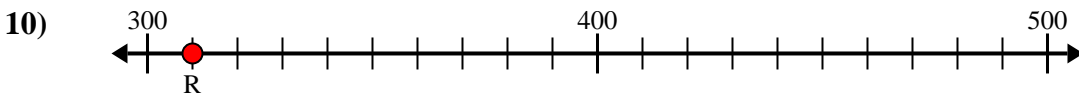
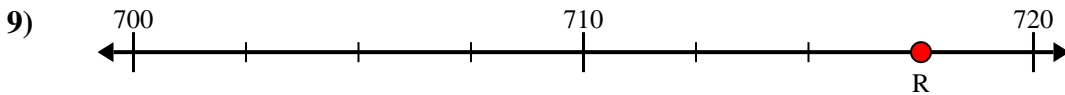
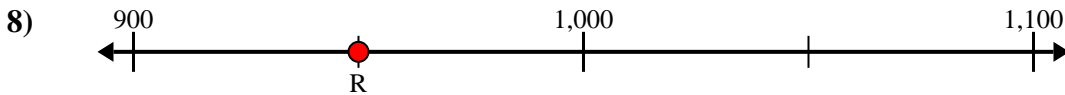
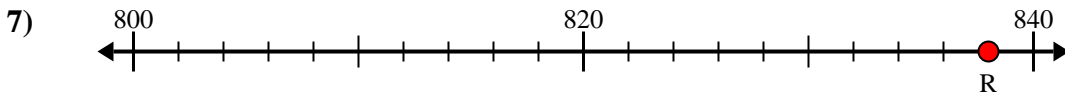
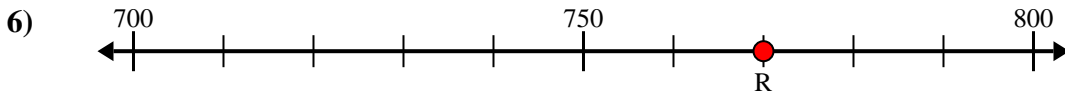
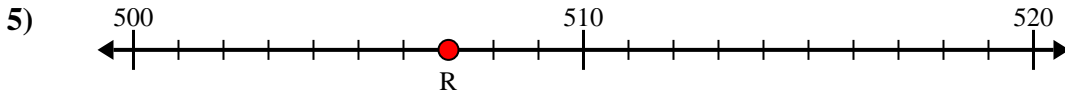
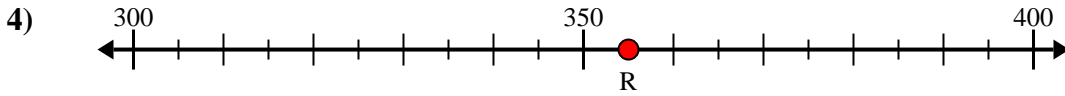
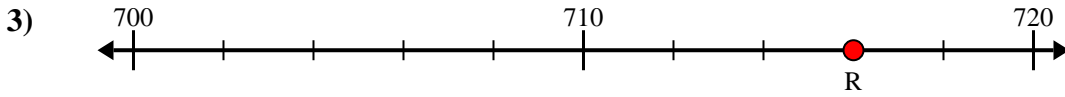


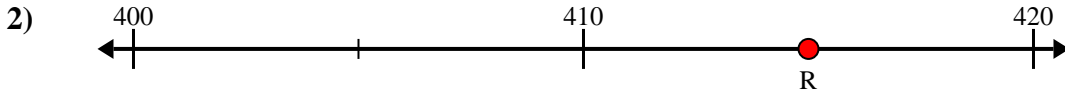

Encontrar el valor de R.

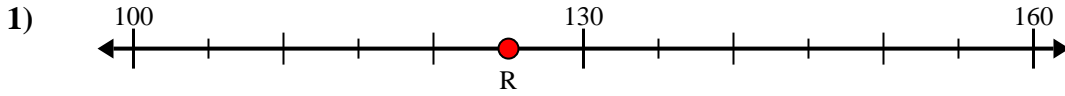

Respuestas

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Encontrar el valor de R.

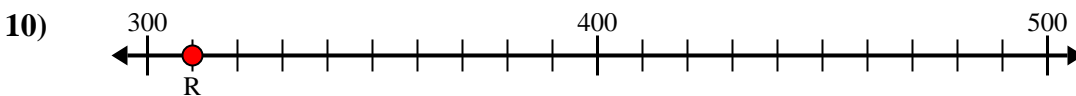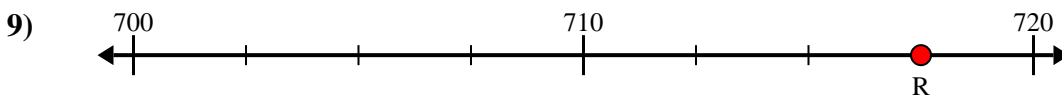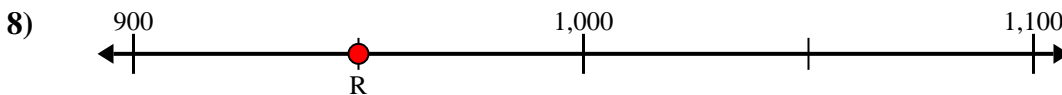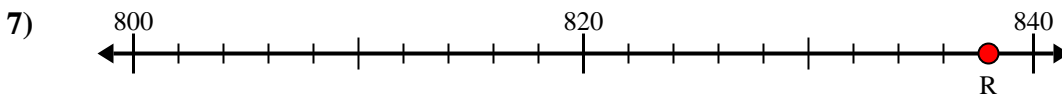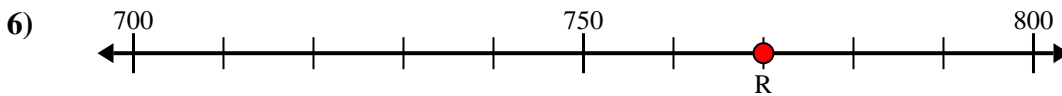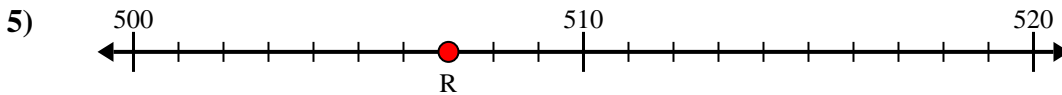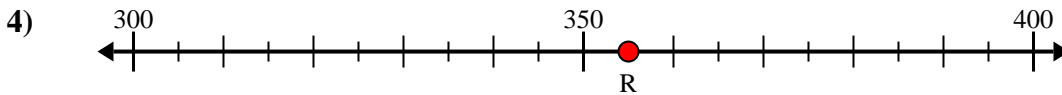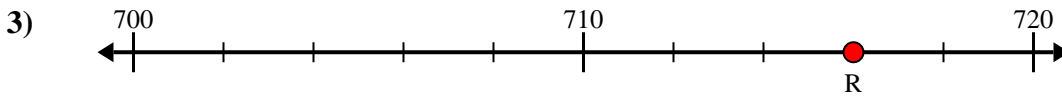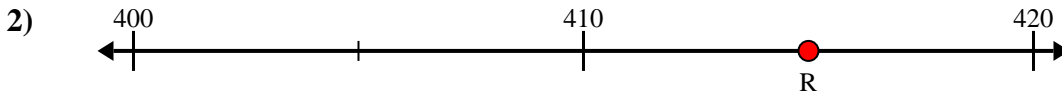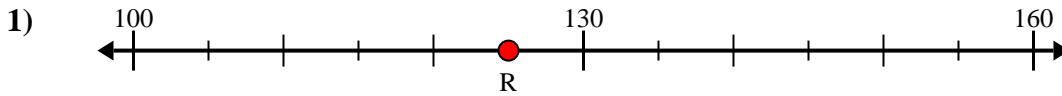

Respuestas

1. 125

2. 415

3. 716

4. 355

5. 507

6. 770

7. 838

8. 950

9. 717.5

10. 310